

Inf2C - Computer Systems

Lecture 10-11

Logic Design

Vijay Nagarajan

School of Informatics
University of Edinburgh




Logic design overview

Binary digital logic circuits:

- Two voltage levels (ground and supply voltage) for 0 and 1
 - Built from transistors used as on/off switches
 - Digital logic with more than two states is not practical

 
Combinational logic: output depends only on the current inputs
(no memory of past inputs)



Sequential logic: output depends on the current inputs as well as
(some) previous inputs → requires “memory”

Combinational logic circuits

 - Inverter (or NOT gate): 1 input and 1 output
“invert the input signal”




IN	OUT
0	1
1	0

$$\text{OUT} = \overline{\text{IN}}$$

Truth table

Combinational logic circuits

 
- Inverter (or NOT gate): 1 input and 1 output
“invert the input signal”



IN	OUT
0	1
1	0

$$\text{OUT} = \overline{\text{IN}}$$

 - AND gate: 2 inputs and 1 output
“output 1 only if both inputs are 1”




IN_1	IN_2	OUT
0	0	0
0	1	0
1	0	0
1	1	1

$$\text{OUT} = \text{IN}_1 \cdot \text{IN}_2$$


Combinational logic circuits

 - OR gate: “output 1 if at least one input is 1”




IN ₁	IN ₂	OUT
0	0	0
0	1	1
1	0	1
1	1	1
 
$$\text{OUT} = \text{IN}_1 + \text{IN}_2$$




Combinational logic circuits

- OR gate: “output 1 if at least one input is 1”

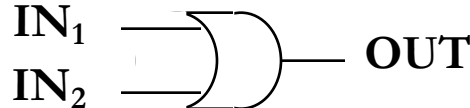
	IN ₁	IN ₂	OUT	$\text{OUT} = \text{IN}_1 + \text{IN}_2$
	0	0	0	
	0	1	1	
	1	0	1	
	1	1	1	

- NOR gate: “output 1 if no input is 1” (NOT OR)

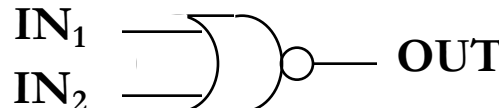	IN ₁	IN ₂	OUT	$\text{OUT} = \overline{\text{IN}_1 + \text{IN}_2}$
	0	0	1	
	0	1	0	
	1	0	0	
	1	1	0	


Combinational logic circuits

- AND gate: “output 1 if both inputs are 1”

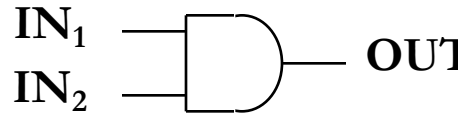	IN ₁	IN ₂	OUT
	0	0	0
	0	1	0
	1	0	0
	1	1	1

OUT = IN₁ . IN₂


- NAND gate: “output 1 if both inputs are not 1” (NOT AND)

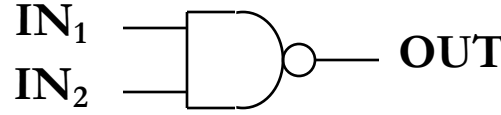	IN ₁	IN ₂	OUT
	0	0	1
	0	1	1
	1	0	1
	1	1	0


OUT = $\overline{\text{IN}_1 \cdot \text{IN}_2}$

Combinational logic circuits

- Multiple-input gates:

 

$OUT = 1$ if all $IN_i = 1$

 


$OUT = 1$ if any $IN_i = 1$

Combinational logic circuits

- Functional completeness:
 - Set of gates that is sufficient to express any boolean function
- Examples of functionally-complete sets of gates:
 - AND + OR + NOT
 - NAND
 - NOR

Multiplexer (mux)

 - Multiplexer: a circuit for selecting one of multiple inputs



$$z = \begin{cases} i_0 & \text{iff } c=0 \\ i_1 & \text{iff } c=1 \end{cases}$$

c	i ₀	i ₁	z
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

$$z = \bar{c}.i_0.\bar{i}_1 + \bar{c}.i_0.i_1 + c.\bar{i}_0.i_1 + c.i_0.i_1$$


$$= \bar{c}.i_0.(\bar{i}_1 + i_1) + c.(\bar{i}_0 + i_0).i_1$$

$$= \bar{c}.i_0 + c.i_1 \quad \text{minimized}$$

“sum of products form”

A multiplexer implementation

 
- Sum of products form: $i_1 \cdot c + i_0 \cdot \overline{c}$
 - Can be implemented with 1 inverter, 2 AND gates & 1 OR gate:



- Sum of products is not practical for circuits with large number of inputs (n)
 - The number of possible products can be proportional to 2^n

Arithmetic circuits

- 32-bit adder

 


64 inputs \rightarrow too complex for
sum of products

- Idea: modularize!
 - Design a generic 1-bit adder block
 - Replicate it N number of times for an N-bit adder


Arithmetic circuits

- 32-bit adder

 

64 inputs \rightarrow too complex for
sum of products

- Full adder:

 


$$\text{sum} = \bar{a}.\bar{b}.c + \bar{a}.b.\bar{c} + a.\bar{b}.\bar{c} + a.b.c$$

$$\text{carry} = b.c + a.c + a.b$$

a	b	c	carry	sum
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Ripple carry adder

- 32-bit adder: chain of 32 full adders

 


- Carry bits c_i are computed in sequence c_1, c_2, \dots, c_{32} (where $c_{32} = s_{32}$), as c_i depends on c_{i-1}
- Since sum bits s_i also depend on c_i , they too are computed in sequence

Propagation delays

- Propagation delay = time delay between input signal change and output signal change at the other end
- Delay depends on:
 1. technology (transistor parameters, wire capacitance, etc.)
 2. delay through each gate (function of gate type)
 3. number of gates driven by a gate's output (**fan out**)
- e.g.: 2-input mux: NOT \rightarrow AND \rightarrow OR \rightarrow 3 gate delays. Fast!
- What's the delay of a 32-bit ripple carry adder?
 - 65 gate delays \rightarrow slow
 - AND2 + OR3 for each of 31 carries to propagate; followed by NOT + AND3 + OR4 for S_{31}

Combinational logic: summary

 
Combinational logic: output depends only on the current inputs



- Does not “remember” previous inputs or outputs

Memory is needed for more complex operations

Sequential logic circuits

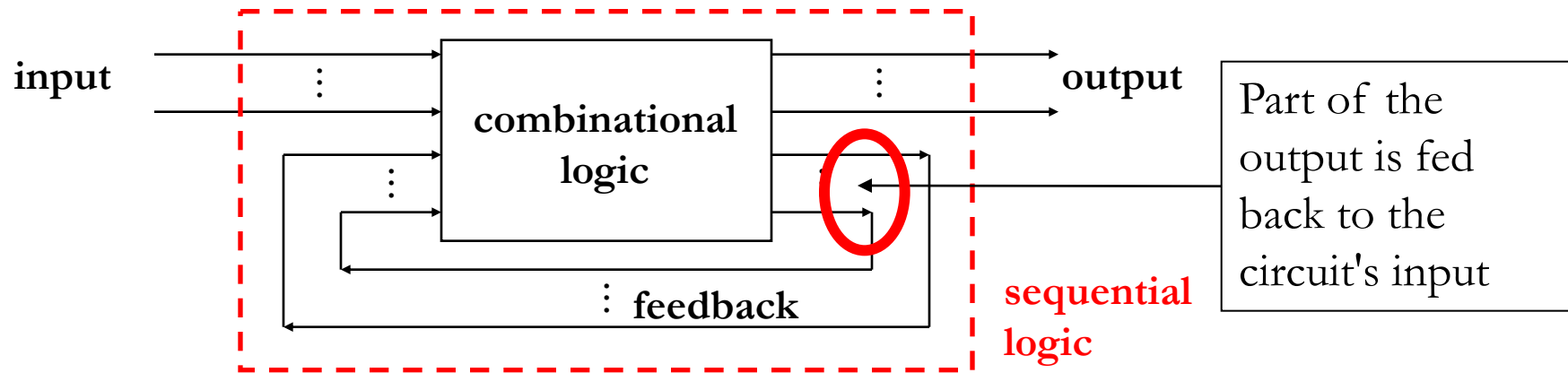


- Output depends on current and (some of the) past inputs
 - The circuit has memory
- Sequences of inputs generate sequences of outputs \Rightarrow


Sequential logic

- With n feedback signals \rightarrow up to 2^n states

Sequential circuit: OR with feedback

 


Sequential circuit: OR with feedback

 

IN	FB	OUT
0	0	0
0	1	1
1	0	1
1	1	1


$$\text{OUT} = \text{IN} + \text{FB}$$

Sequential circuit: OR with feedback

 


- Initial state: both IN and OUT are 0

Sequential circuit: OR with feedback

 


- Initial state: both IN and OUT are 0
- Let's set IN to 1

Sequential circuit: OR with feedback

 


- Initial state: both IN and OUT are 0
- Let's set IN to 1
 - OUT becomes 1

Sequential circuit: OR with feedback

 


- Initial state: both IN and OUT are **0**
- Let's set IN to **1**
 - OUT and FB become **1**

Sequential circuit: OR with feedback

 


- Initial state: both IN and OUT are **0**
- Let's set IN to **1**
 - OUT and FB become **1**
- Let's set IN to **0**

Sequential circuit: OR with feedback

 


- Initial state: both IN and OUT are **0**
- Let's set IN to **1**
 - OUT and FB become **1**
- Let's set IN to **0**
 - OUT does not change.

Sequential circuit: OR with feedback

 


- Initial state: both IN and OUT are **0**
- Let's set IN to **1**
 - OUT and FB become **1**
- Let's set IN to **0**
 - OUT does not change. How to change OUT?

Sequential circuit: OR with feedback

 

- Initial state: both IN and OUT are **0**
- Let's set IN to **1**
 - OUT and FB become **1**
- Let's set IN to **0**
 - OUT does not change. OUT will never change!

Sequential circuit: OR with feedback

 


- Initial state: both IN and OUT are 0
- Let's set IN to 1
 - OUT and FB become 1
- Let's set IN to 0
 - OUT does not change. OUT will never change!


This circuit 'remembers' if there was 1 on IN

Works only once, no reset. Not very practical.

More practical sequential circuits

 


A	B	
0	0	1
0	1	0
1	0	0
1	1	0



- 2 NOR gates
- $OUT_1 = FB_2$; $OUT_2 = FB_1$


More practical sequential circuits

 

A	B	
0	0	1
0	1	0
1	0	0
1	1	0

- Initial state: IN_1 , IN_2 , OUT_2 are 0


More practical sequential circuits

 

A	B	
0	0	1
0	1	0
1	0	0
1	1	0

- Initial state: IN_1 , IN_2 , OUT_2 are 0
- Let's set IN_2 to 1


More practical sequential circuits

 

A	B	
0	0	1
0	1	0
1	0	0
1	1	0

- Initial state: IN_1 , IN_2 , OUT_2 are 0
- Let's set IN_2 to 1


More practical sequential circuits

 


A	B	
0	0	1
0	1	0
1	0	0
1	1	0

- Initial state: IN_1 , IN_2 , OUT_2 are 0
- Let's set IN_2 to 1
 - Nothing changes!

More practical sequential circuits

 


A	B	
0	0	1
0	1	0
1	0	0
1	1	0



- Initial state: IN_1 , IN_2 , OUT_2 are 0
- Let's set IN_2 to 1
 - Nothing changes!
 - In this state, IN_2 does not affect anything


More practical sequential circuits

 

A	B	
0	0	1
0	1	0
1	0	0
1	1	0

- Initial state: IN_1 , IN_2 , OUT_2 are 0


More practical sequential circuits

 


A	B	
0	0	1
0	1	0
1	0	0
1	1	0

- Initial state: IN_1 , IN_2 , OUT_2 are 0
- Let's set IN_1 to 1


More practical sequential circuits

 

A	B	
0	0	1
0	1	0
1	0	0
1	1	0

- Initial state: IN_1 , IN_2 , OUT_2 are 0
- Let's set IN_1 to 1
 - $OUT_1 \Rightarrow 0$


More practical sequential circuits

 

A	B	
0	0	1
0	1	0
1	0	0
1	1	0

- Initial state: IN_1 , IN_2 , OUT_2 are 0
- Let's set IN_1 to 1
 - $OUT_1 \Rightarrow 0$
 - $FB_2 \Rightarrow 0$


More practical sequential circuits

 

A	B	
0	0	1
0	1	0
1	0	0
1	1	0

- Initial state: IN_1 , IN_2 , OUT_2 are 0
- Let's set IN_1 to 1
 - $OUT_1 \Rightarrow 0$
 - $FB_2 \Rightarrow 0$
 - $OUT_2 \Rightarrow 1$


More practical sequential circuits

 

A	B	
0	0	1
0	1	0
1	0	0
1	1	0

- Initial state: IN_1 , IN_2 , OUT_2 are 0
- Let's set IN_1 to 1
 - $OUT_1 \Rightarrow 0$
 - $FB_2 \Rightarrow 0$
 - $OUT_2 \Rightarrow 1$
 - $FB_1 \Rightarrow 1$


More practical sequential circuits

 

A	B	
0	0	1
0	1	0
1	0	0
1	1	0

- Initial state: IN_1, IN_2, OUT_2 are 0
- Let's set IN_1 to 1
 - $OUT_1 \Rightarrow 0$
 - $FB_2 \Rightarrow 0$
 - $OUT_2 \Rightarrow 1$
 - $FB_1 \Rightarrow 1$
- Set IN_1 back to 0

More practical sequential circuits

 

A	B	
0	0	1
0	1	0
1	0	0
1	1	0

- Initial state: IN_1, IN_2, OUT_2 are 0

- Let's set IN_1 to 1

- $OUT_1 \Rightarrow 0$

- $FB_2 \Rightarrow 0$



- $OUT_2 \Rightarrow 1$

- $FB_1 \Rightarrow 1$

- Set IN_1 back to 0



- Nothing changes!

More practical sequential circuits

  


- Initial state: IN₁, IN₂, OUT₂ are 0
- Let's set IN₁ to 1
 - OUT₁ => 0
 - FB₂ => 0
 - OUT₂ => 1
 - FB₁ => 1
- Set IN₁ back to 0
 - Nothing changes!

More practical sequential circuits

  


- Two “mirrored” stable states

More practical sequential circuits

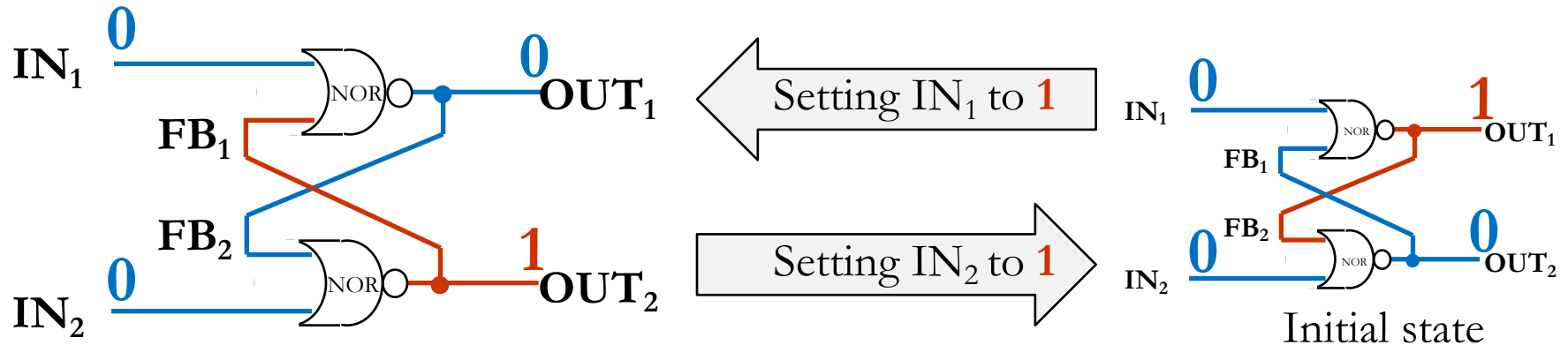


- Two “mirrored” stable states
- Setting one of the inputs to 1 changes the state

More practical sequential circuits

 


- Two “mirrored” stable states
- Setting one of the inputs to 1 changes the state
- Outputs are inverse of each other ($OUT_1 = \overline{OUT_2} = Q$)

More practical sequential circuits

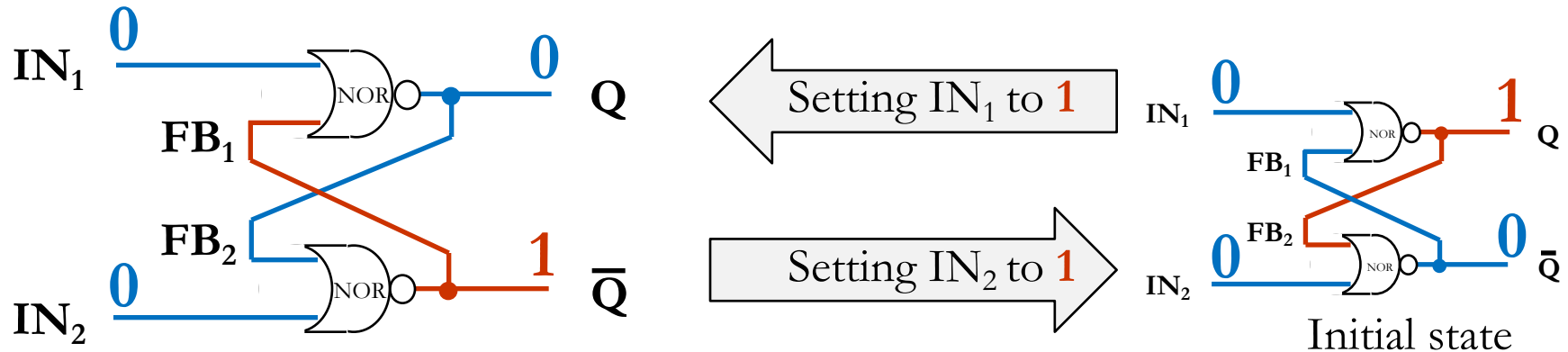

- Two “mirrored” stable states
- Setting one of the inputs to 1 changes the state
- Outputs are inverse of each other ($OUT_1 = \overline{OUT_2} = Q$)


More practical sequential circuits

 

- Two “mirrored” stable states
- Setting one of the inputs to 1 changes the state
- Outputs are inverse of each other ($OUT_1 = \overline{OUT_2} = Q$)

By setting one of the inputs, Q can be set to either 1 or 0

More practical sequential circuits

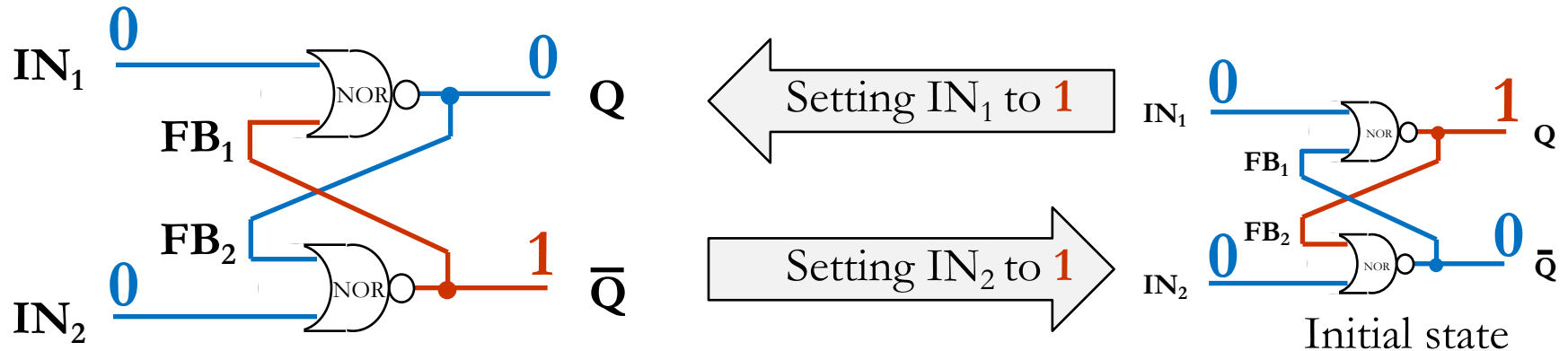


- Two “mirrored” stable states
- Setting one of the inputs to 1 changes the state
- Outputs are inverse of each other ($OUT_1 = \overline{OUT_2} = Q$)

By setting one of the inputs, Q can be set to either 1 or 0

- Setting IN_1 to 1 *resets* the value Q (1 -> 0)
- Setting IN_2 to 1 *sets* the value Q (0 -> 1)

More practical sequential circuits

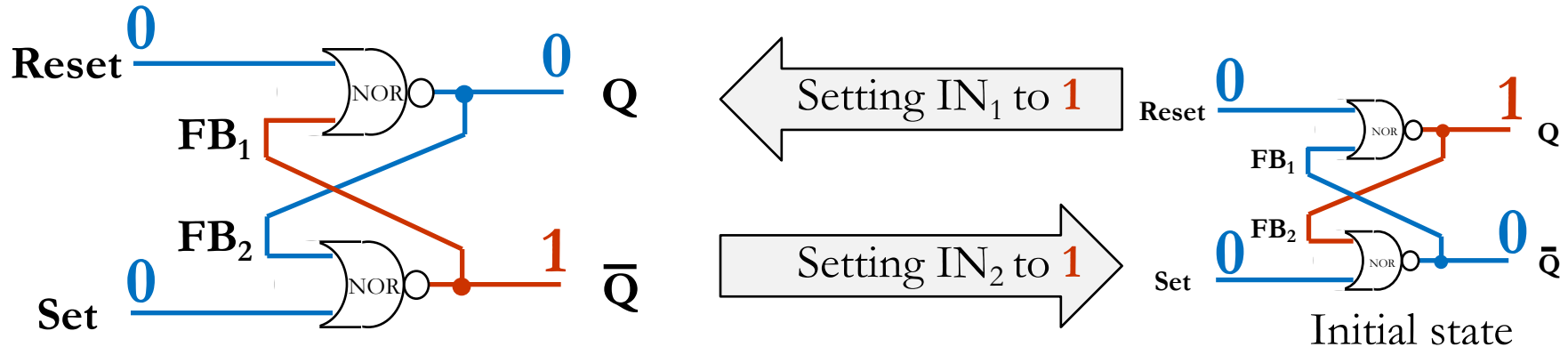


- Two “mirrored” stable states
- Setting one of the inputs to 1 changes the state
- Outputs are inverse of each other ($OUT_1 = \overline{OUT_2} = Q$)

By setting one of the inputs, Q can be set to either 1 or 0

- Setting IN₁ to 1 *resets* the value Q (1 → 0)
- Setting IN₂ to 1 *sets* the value Q (0 → 1)

SR latch


 


S	R	Q_i
0	0	Q_{i-1} ← Previous value
0	1	0
1	0	1
1	1	inv

inv=invalid


Usage: 1-bit memory

  - Keep the value in memory by maintaining $S=0$ and $R=0$
- Set the value in memory to 0 (or 1) by setting $R=1$ (or $S=1$) for a short time




Timing of events

 - Asynchronous sequential logic
 - State (and possibly output) of circuit changes whenever inputs change



Timing of events

 
- Asynchronous sequential logic
 - State (and possibly output) of circuit changes whenever inputs change



 
Problem: different delays on different circuit paths

Timing of events

- Asynchronous sequential logic
 - State (and possibly output) of circuit changes whenever inputs change




 Problem: different delays on different circuit paths




Timing of events

 - Asynchronous sequential logic
 - State (and possibly output) of circuit changes whenever inputs change




 Problem: different delays on different circuit paths




Timing of events

 - Asynchronous sequential logic
 - State (and possibly output) of circuit changes whenever inputs change




 Problem: different delays on different circuit paths





Timing of events

 - **Asynchronous** sequential logic
 - State (and possibly output) of circuit changes whenever inputs change



  
Problem: different delays on different circuit paths



Timing of events

- **Asynchronous** sequential logic

 
- State (and possibly output) of circuit changes whenever inputs change



 Problem: different delays on different circuit paths



- **Solution: Synchronous** sequential logic

- State (and possibly output) can only change at times synchronized to an external signal → the **clock**




Timing of events

Synchronous sequential logic

 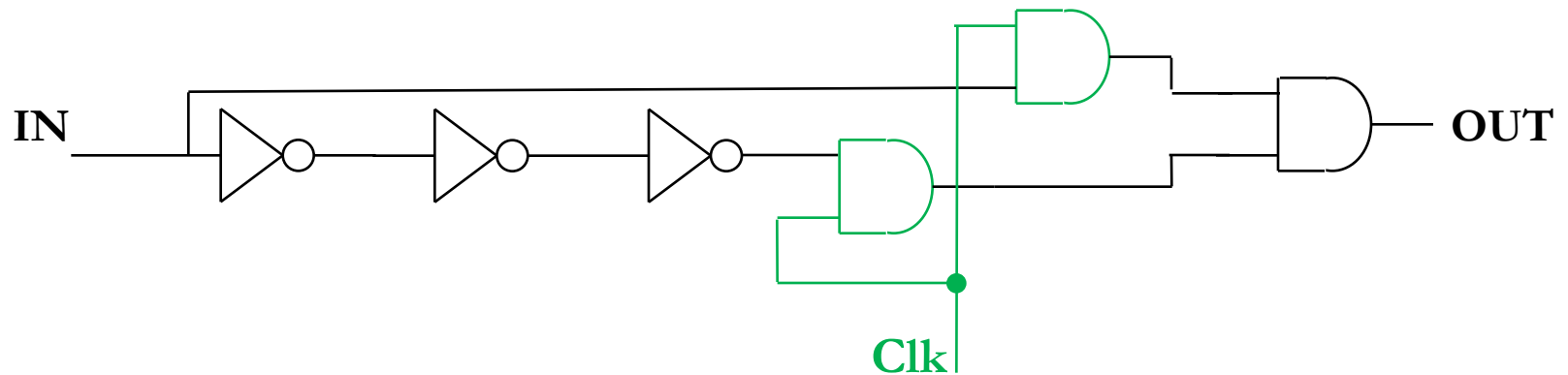


Timing of events

Synchronous sequential logic

 

No Glitches!

Clocked SR latch

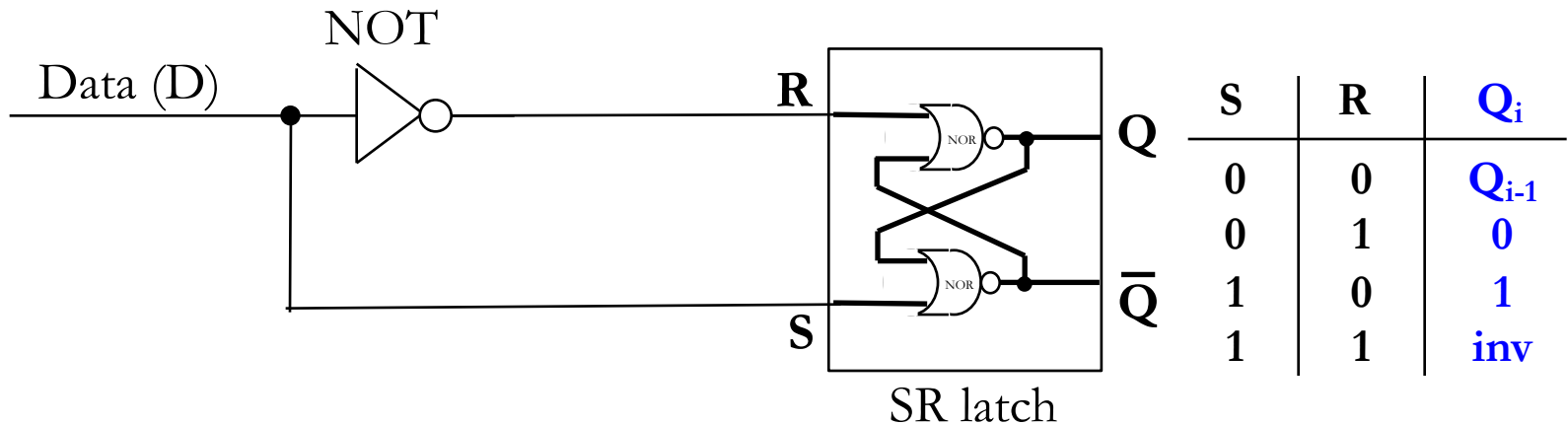

Some logic computes the data (1 bit)


We want to 'save' the data in an SR latch when the data is ready

Problem: glitches

Solution: add clock!



Clocked SR latch

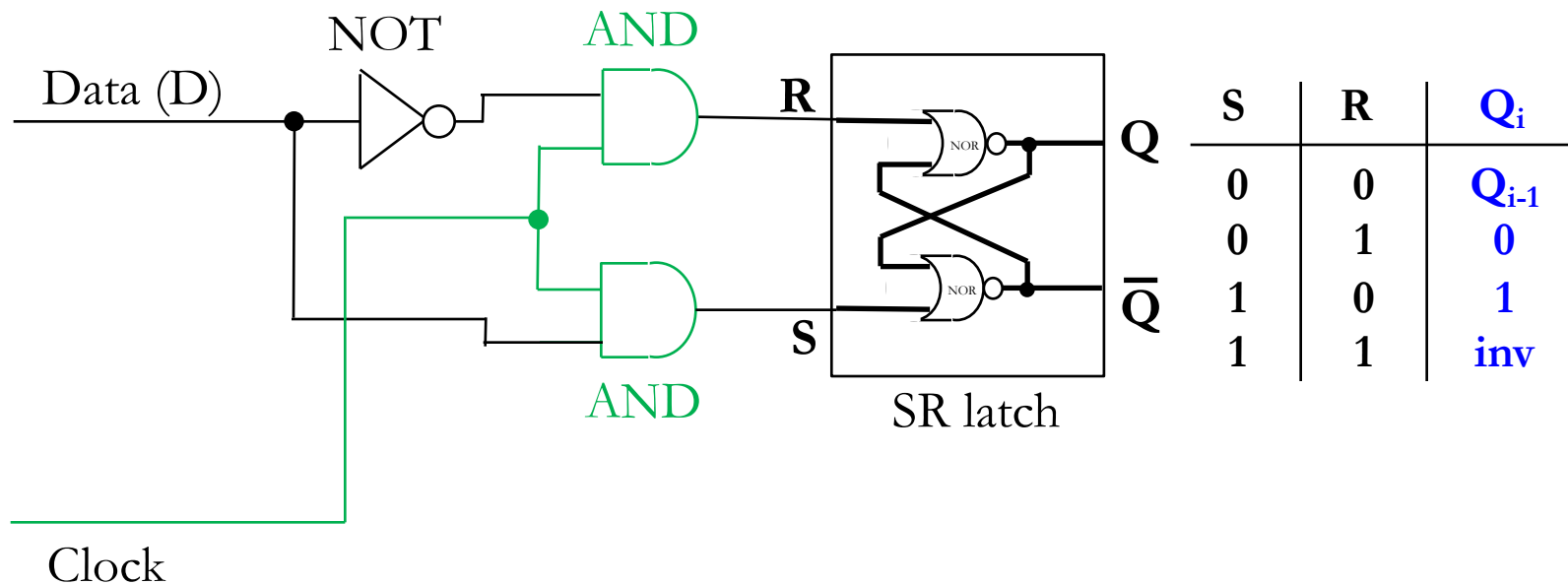


Some logic computes the data (1 bit)

We want to 'save' the data in an SR latch when the data is ready


Set Q to D when Clock is 1; Ignore D if Clock is 0

Clocked SR latch: D flip-flop


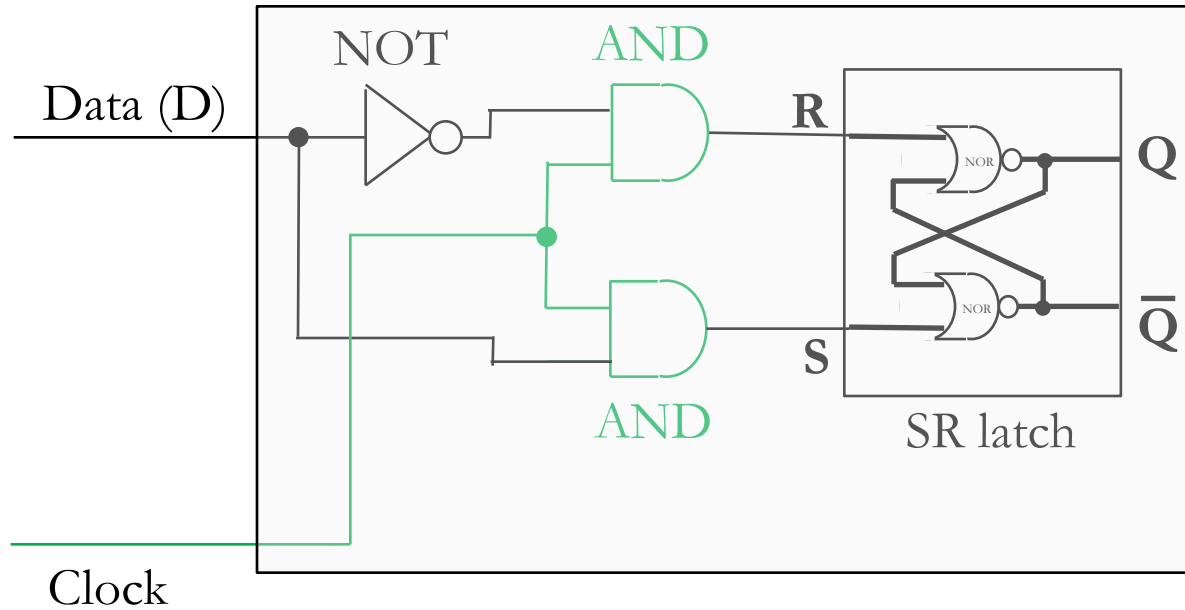


S	R	Q_i
0	0	Q_{i-1}
0	1	0
1	0	1
1	1	inv

D flip-flop


 


Using clock to build a memory element

  


- **Level-triggered D flip-flop:** whenever clock is 1, D is propagated to Q

Using clock to build a memory element


 
 


 - **Level-triggered D flip-flop:** whenever clock is 1, D is propagated to Q
- **Edge-triggered D flip-flop:** on a **positive clock edge**, D is propagated to Q




Register

   - Tie multiple D flip-flops together using a common clock
- E.g., 4-bit register:



[PDF] 4-Bit D-Type Registers With 3-Stat
www.ti.com/lit/gpn/SN74LS173A ▼
50 MHz description. The '173 and 'LS173A 4-bit regi
3-state outputs capable of driving highly capacitive.

General sequential logic circuit

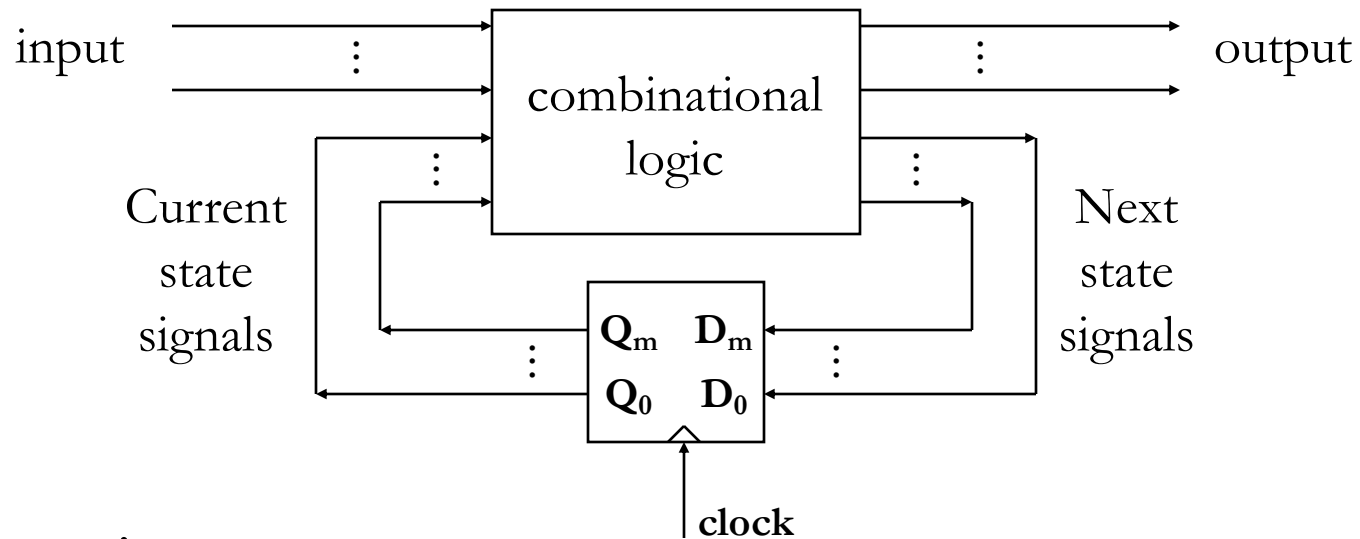


■ Operation:

- At every rising clock edge, next state signals are propagated to current state signals
- Current state signals plus inputs work through combinational logic and generate output and next state signals


Hardware FSM

 - A sequential circuit is a (deterministic) Finite State Machine – FSM
- Example: Vending machine
 - Accepts 10p, 20p coins, sells one product costing 30p, no change given
 - Coin reader has 2 signals: a , b for 10p, 20p coins respectively. These are the inputs to our FSM
 - Output z asserted when 30p or more has been paid in



FSM implementation

 - Methodology:
 - Choose encoding for states, e.g $S_0=00$, ..., $S_3=11$
 - Build truth table for the next state s_1' , s_0' and output z
 - Generate logic equations for s_1' , s_0' , z
 - Design comb logic from logic equations and add state-holding register



s_1	s_0	a	b	s_1'	s_0'	z
0	0	0	0	0	0	0
0	0	0	1	1	0	0
0	0	1	0	0	1	0
0	1	0	0	0	1	0
0	1	0	1	1	1	1
0	1	1	0	1	0	0
.....					